 


## Chapter 06

### Sequential logic

Sequential circuit: A sequential circuit consists of a combinational circuit with memory elements to form a feedback path. These memory elements are capable of storing binary information. The stored binary information defines the state of sequential circuit. Sequential circuit receives information from external input along with the present state of memory elements it determines the output.






## Flip-flop (FF):

A flip-flop ~~circuit~~ circuit can maintain a binary state indefinitely (as long as power is delivered to the circuit) until directed by an input signal to switch states.

Basic FF circuit: A FF circuit can be constructed from two NAND or two NOR gate.

R (Reset)

 

Indeterminate state  $\rightarrow$

~~S=0~~  
~~S=1~~  
R=1

S	R	Q	Q'
1	0	1	0
0	0	1	0
0	1	0	1
0	0	0	1
1	1	0	0


Indeterminate state  $\rightarrow$

(after  $S=1, R=0$ )  
(after  $S=0, R=1$ )

NOR		
A	B	F
0	0	1
0	1	0
1	0	0
1	1	0



# clocked RS flip flop

 


## characteristics table

Q	S	R	Q(t+1)
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	X
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	X

$S=R=1 =$   
Indeterminate

Indeterminate  
state




 

Handwritten truth table for the SR flip-flop:

SR	00	01	11	10
0	0	0	X	1
1	1	0	X	1

$$Q(t+1) = S + QR'$$

 

- ① When both inputs are 0 ( $R=0, S=0$ ), then  $Q(t+1) = Q$ .
- ②  $R=0, S=1$ , then  $Q(t+1) = 1$ .
- ③  $R=1, S=0$ , then  $Q(t+1) = 0$ , state



## JK flipflop

~~FF~~

① JK flipflop is the refinement of RS flipflop because the indeterminate state is removed

② For  $J=1, K=1$  the flip flop switches to its complement state.

if  $Q=1$ , it becomes 0 or  
if  $Q=0$ , it becomes 1.

~~③ Two level J:~~


③ The letter J is for set and K is for clear.

④ The output Q is ANDed with K and CP input so that the flip flop is cleared during a clock pulse only if Q is previously 1.



④

⑤ Similarly for  $Q'$  is ANDed with J.

 

$Q$	$J$	$K$	$Q(t+1)$
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0





Q \ JK	00	01	11	10
0	0	0	1	1
1	1	0	0	1


\* if  $J=0, K=0$  then  $Q(t+1) = Q(t)$

\* if  $J=0, K=1$ , then  $Q(t+1) = 0$

\* if  $J=1, K=0$ , then  $Q(t+1) = 1$



\* if  $J=1, K=1$ , then  $Q(t+1) = Q(t)$

D flip flop

 




# D flip flop

  

$$Q(t+1) = D$$

Q	D	D'
0	0	0
0	1	1
1	0	0
1	1	1

 



## T flip-flop

### Triggering of FFs

- the state of the FF is switched by a momentary change in the input signal.
- This momentary change is called trigger.
- Clocked FFs are triggered by pulse.
- pulse ~~that~~ start from an initial value of 0, goes momentarily to 1 and after a short time it returns to its initial value 0.
- The time interval from the application of the pulse until the ~~code~~ output transition occurs is a critical factor that needs further investigation.




→ Timing problem can be prevented if outputs of the FFs do not start changing until the pulse input has returned to 0.

→ To ensure such an operation a FF must have propagation delay from input to output in excess of the pulse duration.

→ Very critical to maintain propagation delay.

→ Pulse transition can be used rather than pulse duration.
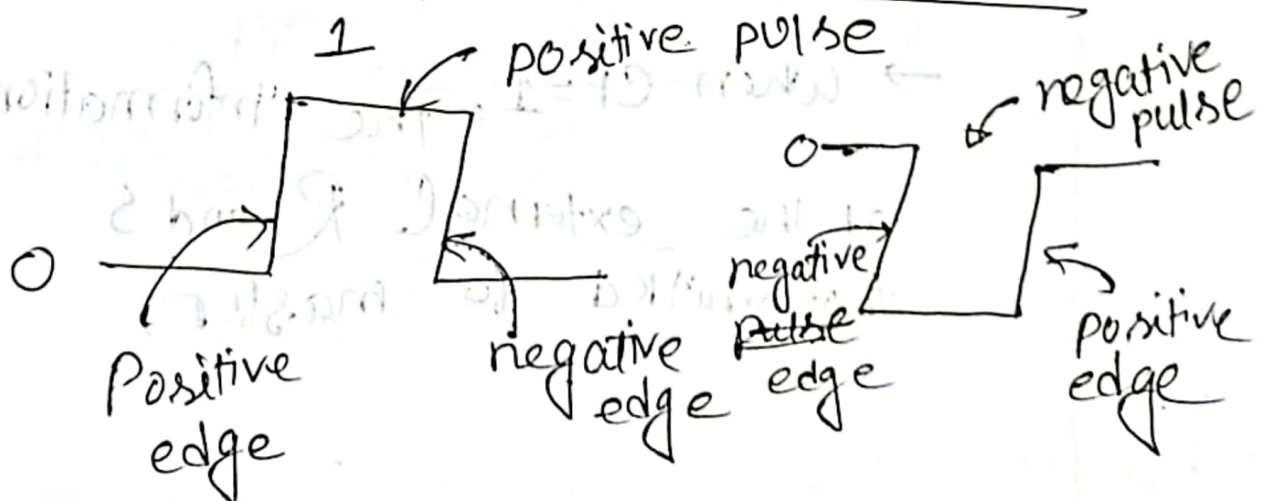
### Positive and negative edge transition





~~at~~ Negative edge trigger


Positive edge trigger

Questions

~~Diff~~ Pulse duration

$CP=1$   
master  
enabled, slave  
disabled

Master-Slave FF

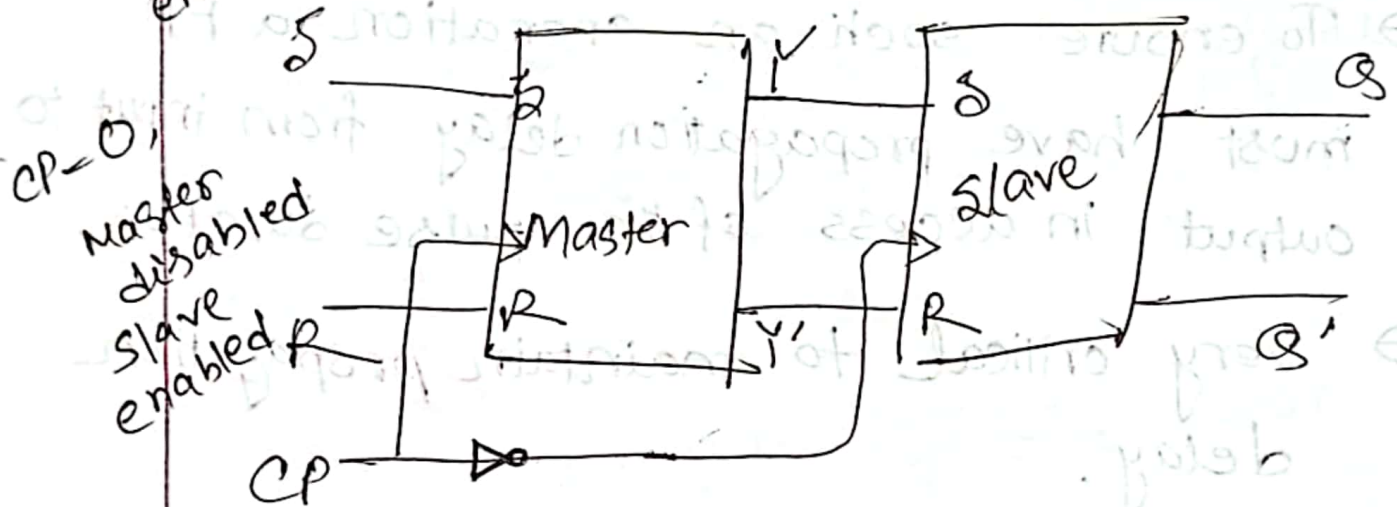

→  $CP=0$ , inverter = 1, output of the slave is 1 so, output  $Q=Y$ ,  $Q'=Y'$ .

→ master is disabled, because  $CP=0$ .

→ When  $CP=1$ , the information at the external R and S transmitted to master,







21/12/23

Present state <u>AB</u>	Next state		Output	
	<u>x=0</u> <u>AB</u>	<u>x=1</u> <u>AB</u>	<u>x=0</u> <u>y</u>	<u>x=1</u> <u>y</u>
0 0	0 0	0 1	0	0
0 1	1 1	0 1	0	0
1 0	1 0	0 0	0	1
1 1	1 0	1 1	0	0

$$A(t) \rightarrow A(t+1) = (A'B + AB' + AB)x' + (AB)x$$

$$B(t) \rightarrow B(t+1) =$$

$$\cancel{B(t)} + (A'B)x' + (A'B' + A'B + AB)x$$

State equation

A state equation is an algebraic expression that specifies the condition for a FF state transition.



## FF Characteristics Table

$S$	$R$	$Q(t+1)$
0	0	$Q(t)$
0	1	0
1	0	1
1	1	?

$J$	$K$	$Q(t+1)$
0	0	$Q(t)$
0	1	0
1	0	1
1	1	$Q'(t)$

$D$	$Q(t+1)$
0	0
1	1

$T$	$Q(t+1)$
0	$Q(t)$
1	$Q'(t)$

## FF Excitation table

During the design process we usually know the transition from present state to next state and we want to find the flip flop ~~cont~~ input condition. For this reason we need a table that lists the required inputs for a given change.





Characteristic table (RS)

$Q(t)$	$S$	$R$	$Q(t+1)$
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	X
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	X

Excitation table		
$Q(t)$	$Q(t+1)$	$S R$
0	0	0 X
0	1	1 0
1	0	0 1
1	1	X 0

Characteristics table (JK) Excitation table

$Q$	$J$	$K$	$Q(t+1)$
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

$Q(t)$	$Q(t+1)$	$J K$
0	0	0 X
0	1	1 X
1	0	X 1
1	1	X 0



mmmm


Design a BCD counter using  
RS flip-flop

Present state

Next state

Present state	Next state	$S_A$	$R_A$	$S_B$	$R_B$	$S_C$	$R_C$	$S_D$	$R_D$
A B C D	A B C D								
0 0 0 0	0 0 0 1	0	x	0	x	0	x	1	0
0 0 0 1	0 0 1 0	0	x	0	x	1	0	0	1
0 0 1 0	0 0 1 1	0	x	0	x	x	0	1	0
0 0 1 1	0 1 0 0	0	x	1	0	0	1	0	1
0 1 0 0	0 1 0 1	0	x	x	0	0	x	1	0
0 1 0 1	0 1 1 0	0	x	x	0	1	0	0	1
0 1 1 0	0 1 1 1	0	x	x	0	x	0	1	0
0 1 1 1	1 0 0 0	1	0	0	1	0	1	0	1
1 0 0 0	1 0 0 1	x	0	0	x	0	x	1	0
1 0 0 1	0 0 0 0	0	1	0	x	0	x	1	1



 

$Q(t)$	$Q(t+1)$	
0	0	0
0	1	1
1	0	0
1	1	1



SA:

		CD			
		00	01	11	10
AB	00	0	0	0	0
	01	0	0	1	0
	11	x	x	x	x
	10	x	0	x	x

$$SA = BCD$$

$$RD = AD$$

$$SB = CD$$

$$RB = D$$

$$SC = A'B$$

$$RC = B$$

$$SD = C'$$


$$RD = C$$



6.23 (JK) - 6.29

6.24 (T)

(2 4 2) → RS flip flop

 

#### 7.4. Ripple counter

##### Binary Ripple Counter

→ A binary ripple counter consists of a series of complementing flip-flops with the output of each flip-flop connected to the CP input of the next higher order flip flop.

— The flip-flop holding the least significant bit receives the incoming count pulses.



~~A<sub>0</sub> A<sub>1</sub> A<sub>2</sub> A~~

A<sub>4</sub> A<sub>3</sub> A<sub>2</sub> A<sub>1</sub> → counts (0 to 15)

0 0 0 0

Modify to make it (0 to 9)

0 0 0 1

0 0 1 0

0 0 1 1

0 0 1 0 0 15

0 0 1 0 1 0


A<sub>4</sub>

A<sub>3</sub>

A<sub>2</sub>

A<sub>1</sub>



Toggled  
Activates  
Next  
flipflop

 

BCD ripple counter (0 to 9) (9 to 0).



# Bcd Ripple Counter

  



\* The FF trigger on negative edge when CP goes from 1 to 0.

\* Output of  $Q_1$  applies to CP input of  $Q_2$  and  $Q_8$  both.

\* Output of  $Q_2$  applies to CP input of  $Q_4$ .

\* CP input goes 1 to 0, the FF is set if  $J=1$ ; is cleared if  $K=1$  and complemented if  $J=K=1$  and left unchanged if  $J=K=0$ .

\* Following conditions:

- 1)  $Q_1$  is complemented on the negative edge of every count pulse.
- 2)  $Q_2$  is complement if  $Q_8=0$ , and  $Q_1$  goes from 1 to 0.



3.  $Q_4$  is complemented when  $Q_2$  goes from 1 to 0.

4.  $Q_8$  is complemented when  $Q_4 Q_2 = 11$  and

$Q_1$  goes from 1 to 0.

$Q_8 = 0, Q_1 = 1 \rightarrow 0$   
 $Q_2 = 1 \rightarrow 0$

$Q_8$	$Q_4$	$Q_2$	$Q_1$
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0
1	0	0	1
0	0	0	0

complement  $Q_1$   
 $J = K = 1$   
 $K = 1$

$Q_8 = 1$